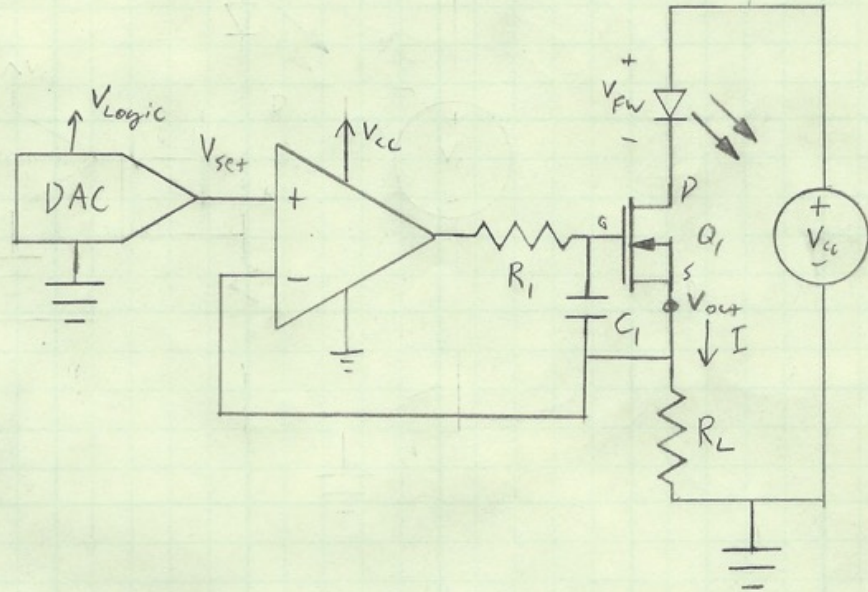


$C_1 = 100\text{nF}$   
Any small ( $< 1\text{MF}$ )  
cap should work  
to slow system &  
compensate miller  
effect to keep  
stability

$R_1$  &  $C_1$  Added for Low speed  
Amplifier stability

$R_1 = 220\ \Omega$  (Any low value  
from  $100\ \Omega$  to  
a few  $100\ \Omega$  will work)



$I = \frac{V_{set}}{R_L} \rightarrow$  OPAMP forces  $V_{set}$  &  $V_{out}$  to be driven  
to the same value by varying the operation  
of  $Q_1$  in triode Region

MAX/Current:

$I_{max} = \frac{V_{logic}}{R_L} \rightarrow$  to make system intrinsically safe

$$R_L = \frac{V_{cc} - V_{FW}}{I_{max}}$$

in General this equation  
will be limiting factor  
for LED, but check  
 $V_{logic}$  equation to make  
sure this